



R6500/R6532 TIMER INTERRUPT PRECAUTIONS

PURPOSE

The R6532 is a RAM, I/O, timer (RIOT) combination device. The timer is an on-board count-down circuit and may be programmed to cause interrupts to the R6502 microprocessor. The timer interrupt is enabled by simply addressing the R6532 with the necessary selects and address bits. It is *not* necessary to load any internal registers to enable the interrupt, only to address the device.

The R6502 (or one of its 28-pin versions) microprocessor can inadvertently cause addressing of the R6532 (or other devices with a timer) during start-up or RESET operations. When \overline{RES} is driven low, the R6502 and R6532 are initialized to known internal states. When \overline{RES} goes high, however, the start-up procedure is initiated and the first two cycles contain arbitrary or random addresses on the bus. Table 1 illustrates the cycles immediately following \overline{RES} going high.

In most cases, this is normally not a problem, since the occurrence of \overline{RES} causes the R6502 \overline{IRQ} interrupt to be disabled. However, if the R6532 interrupt output is connected to the \overline{NMI} (Non-Maskable Interrupt) input of the R6502 and the R6532 timer interrupt is inadvertently enabled during start-up, a timer interrupt may occur before the processor has executed its system initialization procedure. The possibility of all these things happening is somewhat remote, but can be a potential problem.

DESCRIPTION

There are several solutions to this problem:

1. Use the \overline{IRQ} interrupt input of the R6502, instead of \overline{NMI} . In this way, the \overline{IRQ} interrupt is automatically disabled by \overline{RES} and the R6532 timer interrupt cannot occur.
2. Use separate \overline{RES} signals for the R6502 and the R6532. In order to avoid the first two cycles of the start-up (wherein the addresses are unpredictable), it is necessary to hold the \overline{RES} to the 6532 low *after* the \overline{RES} to the R6502 goes high. This is illustrated in Figure 1.

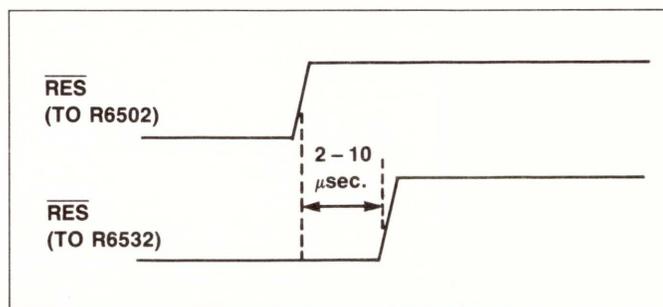


Figure 1. Delayed Reset to R6532

Table 1. Start-Up Cycle

Cycles	Address Bus	Data Bus	External Operation	Internal Operation
1	?	?	Don't Care	Hold during Reset
2	? + 1	?	Don't Care	First Start State
3	0100 + SP	?	Don't Care	Second Start State
4	0100 + SP - 1	?	Don't Care	Third Start State
5	0100 + SP - 2	?	Don't Care	Fourth Start State
6	FFFC	Start PCL	Fetch First Vector	
7	FFFD	Start PCH	Fetch Second Vector	Hold PCL
8	PCH PCL	First OP CODE	Load First OP CODE	

3. Gate the R6532 \overline{IRQ} output to the R6502 \overline{NMI} input with a circuit which is enabled by the initialization routine of the processor. Figure 2 shows a possible configuration, with the gate enabled only when the processor does a write operation with A15 high. Note that this scheme essentially allows disabling of the \overline{NMI} in the R6502.

There are likely to be many other solutions to this problem. These ideas are intended to provide some simple ones and to provoke thought for others from the reader.

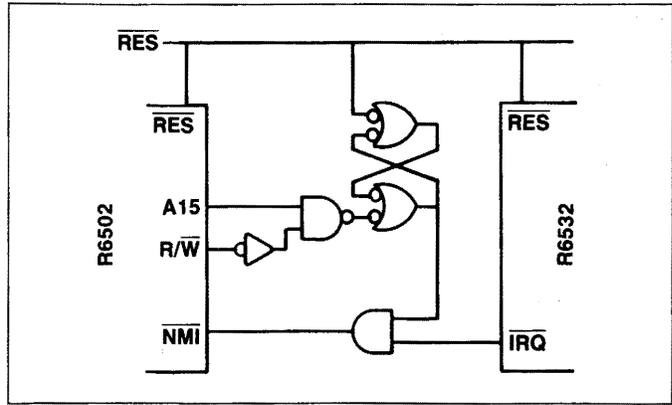


Figure 2. Scheme for Gating to the NMI Input

Information furnished by Rockwell International Corporation is believed to be accurate and reliable. However, no responsibility is assumed by Rockwell International for its use, nor any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of Rockwell International other than for circuitry embodied in a Rockwell product. Rockwell International reserves the right to change circuitry at any time without notice. This document is subject to change without notice.

©Rockwell International Corporation 1984
All Rights Reserved

Printed in U.S.A.

SEMICONDUCTOR PRODUCTS DIVISION REGIONAL ROCKWELL SALES OFFICES

HOME OFFICE

Semiconductor Products Division
Rockwell International
4311 Jamboree Road
P.O. Box C, MS 501-300
Newport Beach, California
92658-8902
(714) 833-4700
TWX: 910 591-1698

UNITED STATES

Semiconductor Products Division
Rockwell International
1842 Reynolds
Irvine, California 92714
(714) 833-4655
TWX: 910 595-2518

Semiconductor Products Division
Rockwell International
3375 Scott Blvd., Suite 410
Santa Clara, California 95054
(408) 980-1900
TLX: 756560

Semiconductor Products Division
Rockwell International
2001 N. Collins Blvd., Suite 103
Richardson, Texas 75080
(214) 996-6500
TLX: 73-307

Semiconductor Products Division
Rockwell International
10700 West Higgins Rd., Suite 102
Rosemont, Illinois 60018
(312) 297-8862
TWX: 910 233-0179 (RI MED ROSM)

Semiconductor Products Division
Rockwell International
5001B Greentree
Executive Campus, Rt. 73
Marlton, New Jersey 08053
(609) 596-0090
TWX: 710 940-1377

FAR EAST

Semiconductor Products Division
Rockwell International Overseas Corp.
Itohia Hiraakawa-cho Bldg.
7-6, 2-chome, Hiraakawa-cho
Chiyoda-ku, Tokyo 102, Japan
(03) 265-8806
TLX: J22198

Rockwell Collins International
Tai Sang Commercial Bldg., 11th Floor
24-34 Hennessy Rd.
Hong Kong
(5) 274-321
TLX: 74071 HK

EUROPE

Semiconductor Products Division
Rockwell International GmbH
Fraunhoferstrasse 11B
D-8033 Munchen-Martinsried
West Germany
(089) 857-6016
TLX: 0521/2650 rimd d

Semiconductor Products Division
Rockwell International Limited
Heathrow House, Bath Rd.
Cranford, Hounslow,
Middlesex, TW5 9QW England
(01) 759-2366
TLX: 851-25463

Semiconductor Products
Rockwell Collins Italiana S.P.A.
Via Boccaccio, 23
20123 Milano, Italy
(02) 498.74.79
TLX: 316562 RCIMIL 1

YOUR LOCAL REPRESENTATIVE